

Ejercicio 3 – Extraordinaria 2 – Curso 20/21

- a) Definir el álgebra de Boole $\mathbb{B}_2^n$ y el orden inducido en ella.
- b) Definir y dibujar un circuito lógico que calcule $(x-4)$ módulo 4, siendo x un entero comprendido entre 0 y 7.

$$b) f: \mathbb{B}_2^m \longrightarrow \mathbb{B}_2^m$$

$$0 = (000)_2$$

$$1 = (001)_2$$

$$2 = (010)_2$$

$$3 = (011)_2$$

$$4 = (100)_2$$

$$5 = (101)_2$$

$$6 = (110)_2$$

$$7 = (111)_2$$

$$f(x) = (x-4) \bmod 4$$

$$\mathbb{Z}_4 = \{ \overline{0}, \overline{1}, \overline{2}, \overline{3} \}$$

$$0 = (00)_2$$

$$1 = (01)_2$$

$$2 = (10)_2$$

$$3 = (11)_2$$

$$f: \mathbb{B}_2^3 \longrightarrow \mathbb{B}_2^2$$

$$f(0) = (0-4) \bmod 4 \equiv (-4) \bmod 4 \equiv 0 \bmod 4 = 0$$

$$-4 = 4 \cdot (-1) + 0$$

$$f(0,0,0) = (0,0)$$

$$f(1) = (1-4) \bmod 4 \equiv (-3) \bmod 4 \equiv 1 \bmod 4 = 1$$

$$-3 = 4 \cdot (-1) + \underline{\underline{1}}$$

$$f(0,0,1) = (0,1)$$

$$f(2) = (2-4) \bmod 4 \equiv (-2) \bmod 4 \equiv 2 \bmod 4 = 2$$

$$-2 = 4 \cdot (-1) + 2$$

$$f(0,1,0) = (1,0)$$

$$f(3) = (3-4) \bmod 4 \equiv -1 \bmod 4 \equiv 3 \bmod 4 = 3$$

$$f(0, 1, 1) = (1, 1)$$

$$f(4) = (4-4) \bmod 4 \equiv 0 \bmod 4$$

$$f(1, 0, 0) = (0, 0)$$

$$f(5) = (5-4) \bmod 4 \equiv 1 \bmod 4$$

$$f(1, 0, 1) = (0, 1)$$

$$f(6) = (6-4) \bmod 4 \equiv 2 \bmod 4$$

$$f(1, 1, 0) = (1, 0)$$

$$f(7) = (7-4) \bmod 4 \equiv 3 \bmod 4$$

$$f(1, 1, 1) = (1, 1)$$

x	y	z	f_1	f_2
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1

$$f_1(x, y, z) = y$$

$$f_2(x, y, z) = z$$

$$f(x, y, z) = (y, z)$$

